

Name – Anupam Sanidhya

Enrolment number – 510817049

Roll number – 42 (Hy)

Assignment 2

1.) Design and simulate the behavioral model of an UP/DOWN counter that is capable of counting up to 10. Use one input count_mode to control the mode of counting i.e. for count_mode = '1' the counter will operate as an UP counter and for count_mode = '0' the counter will behave as a DOWN counter. Use a reset input to reset the counter anytime to 0.

VHDL MODULE:

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_unsigned.ALL;
-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--use IEEE.NUMERIC_STD.ALL;
-- Uncomment the following library declaration if instantiating
-- any Xilinx primitives in this code.
--library UNISIM;
--use UNISIM.VComponents.all;
```

entity Ass2Q1 is

```
Port ( clk : in  STD_LOGIC;

      count_mode : in  STD_LOGIC;

      reset : in  STD_LOGIC;

      counter : out STD_LOGIC_VECTOR(3 downto 0));
```

end Ass2Q1;

architecture Behavioral of Ass2Q1 is

signal c:std_logic_vector(3 downto 0);

begin

process(clk,reset)

begin

if(rising_edge(clk))

then

if(reset='1')

then

c<="0000";

else

if(count_mode='1')

then

if(c="1010")

then

c<="0000";

else

c<=c+x"1";

end if;

else

if(c="0000")

then

c<="1010";

else

c<=c-x"1";

end if;

end if;

end if;

end if;

end process;

```
counter<=c;
end Behavioral;
```

TEST BENCH :

```
LIBRARY ieee;
```

```
USE ieee.std_logic_1164.ALL;
```

```
-- Uncomment the following library declaration if using
```

```
-- arithmetic functions with Signed or Unsigned values
```

```
--USE ieee.numeric_std.ALL;
```

```
ENTITY test IS
```

```
END test;
```

```
ARCHITECTURE behavior OF test IS
```

```
-- Component Declaration for the Unit Under Test (UUT)
```

```
COMPONENT Ass2Q1
```

```
PORT(
```

```
    clk : IN  std_logic;
```

```
    count_mode : IN  std_logic;
```

```
    reset : IN  std_logic;
```

```
    counter : OUT  std_logic_vector(3 downto 0)
```

```
);
```

```
END COMPONENT;
```

```
--Inputs
```

```
signal clk : std_logic := '0';
```

```
signal count_mode : std_logic := '0';
```

```
signal reset : std_logic := '0';
```

```
--Outputs
```

```
signal counter : std_logic_vector(3 downto 0);
```

```
-- Clock period definitions
```

```
constant clk_period : time := 10 ns;
```

```
BEGIN
```

```
-- Instantiate the Unit Under Test (UUT)
```

```
 uut: Ass2Q1 PORT MAP (
```

```
    clk => clk,
```

```
    count_mode => count_mode,
```

```
    reset => reset,
```

```
    counter => counter
```

```
);
```

```
-- Clock process definitions
```

```
clk_process :process
```

```
begin
```

```
    clk <= '0';
```

```
    wait for clk_period/2;
```

```
    clk <= '1';
```

```
    wait for clk_period/2;
```

```
end process;
```

```
-- Stimulus process
```

```
stim_proc: process
```

```
begin
```

```
    -- hold reset state for 100 ns.
```

```
    reset<='1';
```

```
    wait for 200 ns;
```

```
    reset<='0';
```

```
    wait for 300 ns;
```

```
    count_mode<='0';
```

```
    wait for 400 ns;
```

```
    reset<='0';
```

```
    count_mode<='1';
```

```
    wait for clk_period*10;
```

```
    -- insert stimulus here
```

```
    wait;
```

```
end process;
```

```
END;
```

[illegible]

The screenshot shows the ISim (0.40d) software interface. The left pane lists the signals and their current values:

Name	Value
clk	0
count_mode	0
reset	0
counter[3:0]	0101
[3]	0
[2]	1
[1]	0
[0]	1
clk_period	10000 ps

The right pane displays the timing diagram. A yellow cursor is positioned at 261.297 ns. The counter output is 0000, and the clock period is 10000 ps. The diagram shows the clock signal (clk) as a periodic square wave and the counter output (counter[3:0]) as a 4-bit binary value that changes at each clock edge.

2.) Design and simulate the behavioral model of a 4 bit shift register that can support the following modes of data transfer.

- a. Serial in parallel out (SIPO)
- b. Serial in serial out (SISO)
- c. Parallel in serial out (PISO)
- d. Parallel in parallel out (PIPO).

Use case statement for this design. Use one input reg_mode [std_logic_vector (1 downto 0)] to control the nature of behavior of the register. Use “00” for SIPO, “01” for SISO and so on.

VHDL MODULE:

Mux:

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--use IEEE.NUMERIC_STD.ALL;

-- Uncomment the following library declaration if instantiating
-- any Xilinx primitives in this code.
--library UNISIM;
--use UNISIM.VComponents.all;

entity moxx is
  Port ( i0,i1 : in  STD_LOGIC;
        s : in  STD_LOGIC;
        o : out STD_LOGIC);
end moxx;

architecture Behavioral of moxx is

begin
  o<= i0 when s='0' else
    i1 when s='1';

end Behavioral;
```

Barrel Register:

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

-- Uncomment the following library declaration if using
```

```
-- arithmetic functions with Signed or Unsigned values
--use IEEE.NUMERIC_STD.ALL;

-- Uncomment the following library declaration if instantiating
-- any Xilinx primitives in this code.
--library UNISIM;
--use UNISIM.VComponents.all;
```

```
entity shiftregister is
    Port ( mode : in  STD_LOGIC_VECTOR (1 downto 0);
          sout : out  STD_LOGIC;
          sin,clk,e,w_mode : in  STD_LOGIC;
          pout : out  STD_LOGIC_VECTOR (3 downto 0);
          pin : in  STD_LOGIC_VECTOR (3 downto 0));
end shiftregister;
```

```
architecture Behavioral of shiftregister is
    signal d:std_logic_vector(3 downto 0):="0000";
begin
    process(e,clk)
    begin
        if(e='1' and clk'event and clk='1')then
        if(w_mode='1')then
        case mode is
        when "00" | "01" =>
            d(0)<=d(1);
            d(1)<=d(2);
            d(2)<=d(3);
            d(3)<=sin;
        when "10" | "11" =>
            d<=pin;
        when others =>
        end case;
        end if;
        case mode is
        when "01"| "10" =>
            sout <= d(0);
        when "00" | "11" =>
            pout<=d;
        when others =>
        end case;
        end if;
    end process;
end Behavioral;
```

TEST BENCH :

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
```

```
-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--USE ieee.numeric_std.ALL;
```

```
ENTITY test IS
END test;
```

```
ARCHITECTURE behavior OF test IS
```

```
-- Component Declaration for the Unit Under Test (UUT)
```

```
COMPONENT shiftregister
PORT(
    mode : IN  std_logic_vector(1 downto 0);
    sout : OUT  std_logic;
    sin : IN  std_logic;
    clk : IN  std_logic;
    e : IN  std_logic;
    w_mode : IN  std_logic;
    pout : OUT  std_logic_vector(3 downto 0);
    pin : IN  std_logic_vector(3 downto 0)
```

```

);
END COMPONENT;

--Inputs
signal mode : std_logic_vector(1 downto 0) := (others => '0');
signal sin : std_logic := '0';
signal clk : std_logic := '0';
signal e : std_logic := '0';
signal w_mode : std_logic := '0';
signal pin : std_logic_vector(3 downto 0) := (others => '0');

--Outputs
signal sout : std_logic;
signal pout : std_logic_vector(3 downto 0);

-- Clock period definitions
constant clk_period : time := 10 ns;

BEGIN

-- Instantiate the Unit Under Test (UUT)
uut: shiftregister PORT MAP (
    mode => mode,
    sout => sout,
    sin => sin,
    clk => clk,
    e => e,
    w_mode => w_mode,
    pout => pout,
    pin => pin
);

-- Clock process definitions
clk_process :process
begin
    clk <= '0';
    wait for clk_period/2;
    clk <= '1';
    wait for clk_period/2;
end process;


-- Stimulus process
stim_proc: process
begin
    mode <= "00", "01" after 250 ns, "10" after 500 ns, "11" after 750 ns;
    e <= '1', '0' after 250 ns, '1' after 300 ns;
    w_mode <= '0', '1' after 50 ns;
    sin <= '1', '0' after 50 ns, '1' after 100 ns, '0' after 150 ns, '1' after 250 ns;
    pin <= "0000", "0001" after 550 ns, "0010" after 600 ns, "0101" after 650 ns, "1001" after 700 ns, "1101" after 750 ns,
    "0001" after 800 ns, "0010" after 850 ns, "0101" after 900 ns, "1001" after 950 ns, "1101" after 1000 ns;
    -- insert stimulus here

    wait;
end process;


END;

```


RTL Schematic –

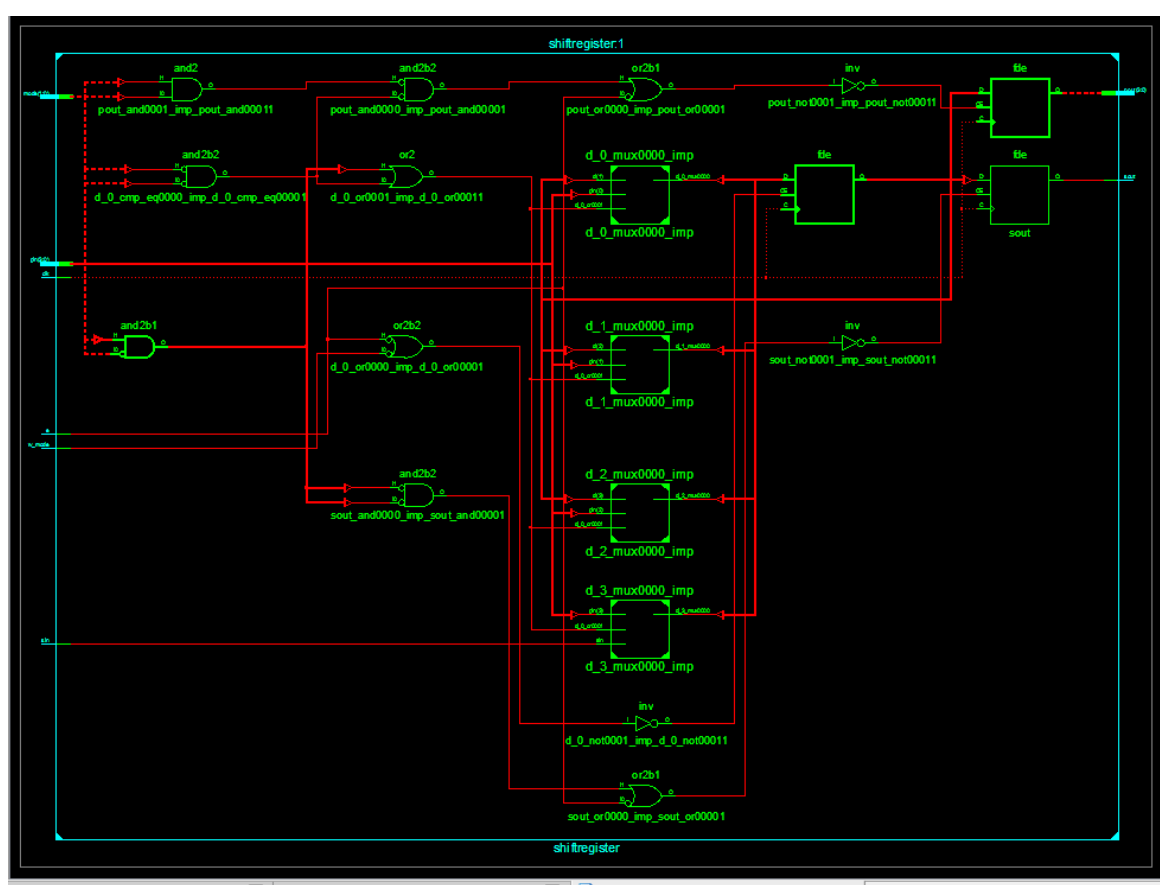

Simulation –

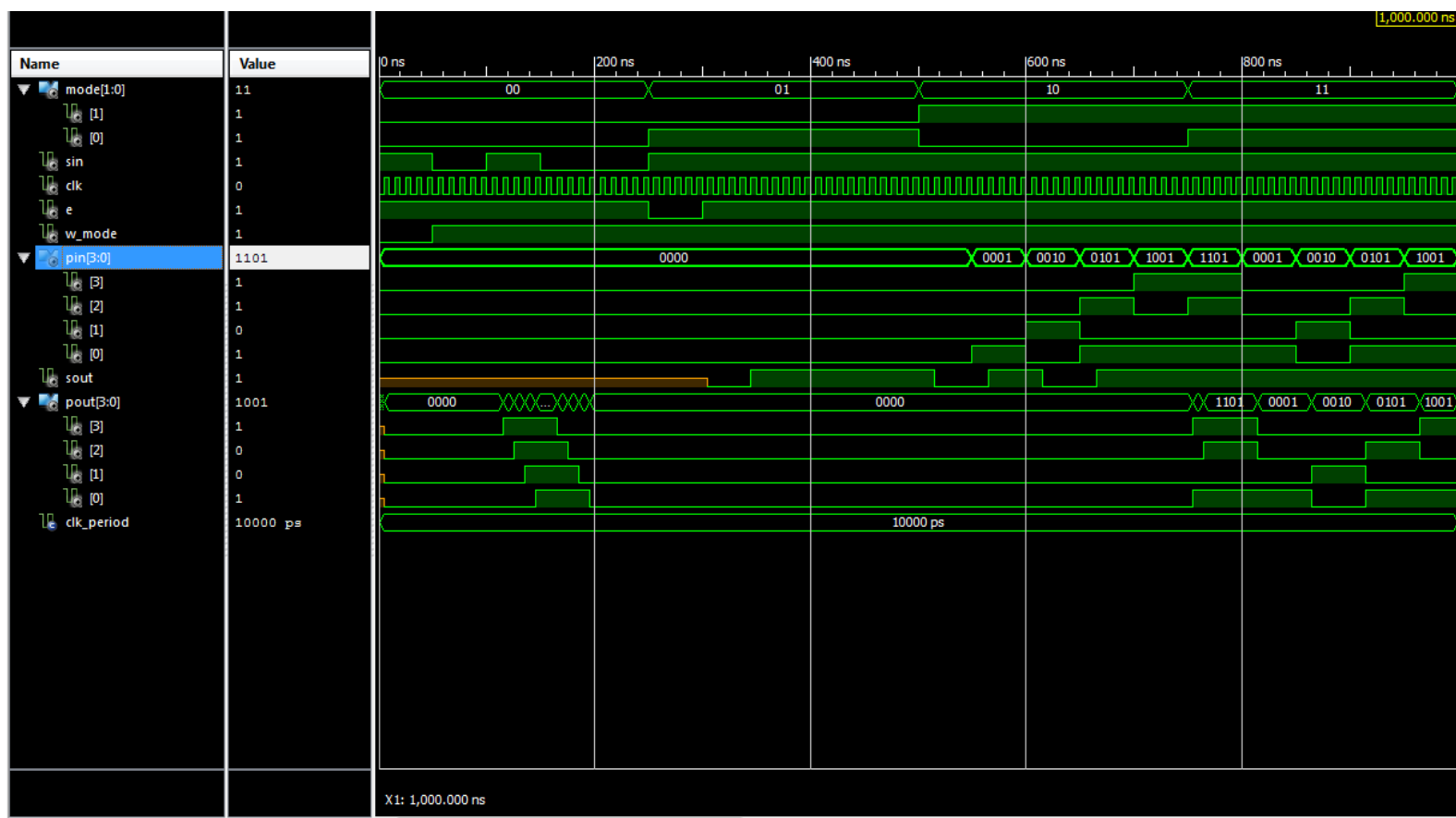

3. Design the followings:

a.) Design and simulate the behavioral model of an 8 bit even parity generator.

VHDL MODULE:

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--use IEEE.NUMERIC_STD.ALL;

-- Uncomment the following library declaration if instantiating
-- any Xilinx primitives in this code.
--library UNISIM;
--use UNISIM.VComponents.all;

entity parity_gen is
    Port ( a : in  STD_LOGIC_VECTOR (7 downto 0);
          b : out STD_LOGIC);
end parity_gen;

architecture Behavioral of parity_gen is

begin

process(a)
begin
b <= a(0) xor a(1) xor a(2) xor a(3) xor a(4) xor a(5) xor a(6) xor a(7);
end process;

end Behavioral;
```

TEST BENCH :

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
ENTITY TEST IS
END TEST;
ARCHITECTURE behavior OF TEST IS
    COMPONENT parity_gen
        PORT(
            a: IN  std_logic_vector(0 to 7);
            b : OUT std_logic_vector(0 to 8)
        );
    END COMPONENT;
    signal a: std_logic_vector(0 to 7) := (others => '0');
```

```

signal b : std_logic_vector(0 to 8);
BEGIN
uut: parity_gen PORT MAP (
    a => a,
    b => b
);
stim_proc: process
begin


a<="00011000";
wait for 50 ns;
a<="10011000";
wait for 50 ns;
a<="01000100";
wait for 50 ns;
a<="10011000";
wait for 50 ns;
a<="10000001";
wait for 50 ns;
a<="00001100";
wait for 50 ns;
a<="11110010";
wait for 50 ns;

    wait;
end process;


END;

```

RTL Schematic –

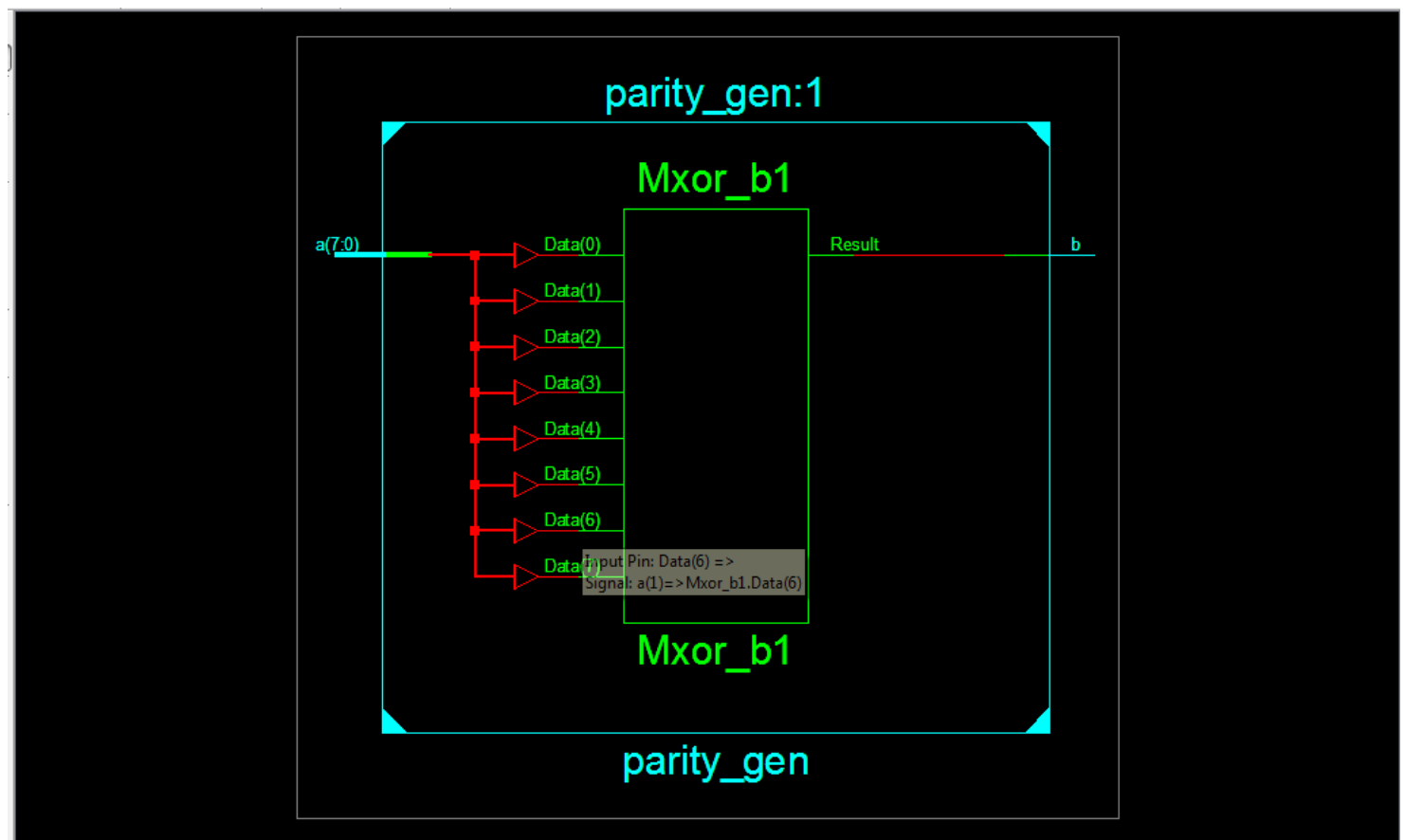

Simulation –

 

b.) Design and simulate the behavioral model an 8 bit even parity checker.

VHDL MODULE:

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--use IEEE.NUMERIC_STD.ALL;

-- Uncomment the following library declaration if instantiating
-- any Xilinx primitives in this code.
--library UNISIM;
--use UNISIM.VComponents.all;

entity parity_chk is
    Port ( a : in  STD_LOGIC_VECTOR (7 downto 0);
          b : in  STD_LOGIC;
          c : out STD_LOGIC);
end parity_chk;


architecture Behavioral of parity_chk is

begin

c <= not (a(0) xor a(1) xor a(2) xor a(3) xor a(4) xor a(5) xor a(6) xor a(7) xor b);

end Behavioral;
```

RTL Schematic –

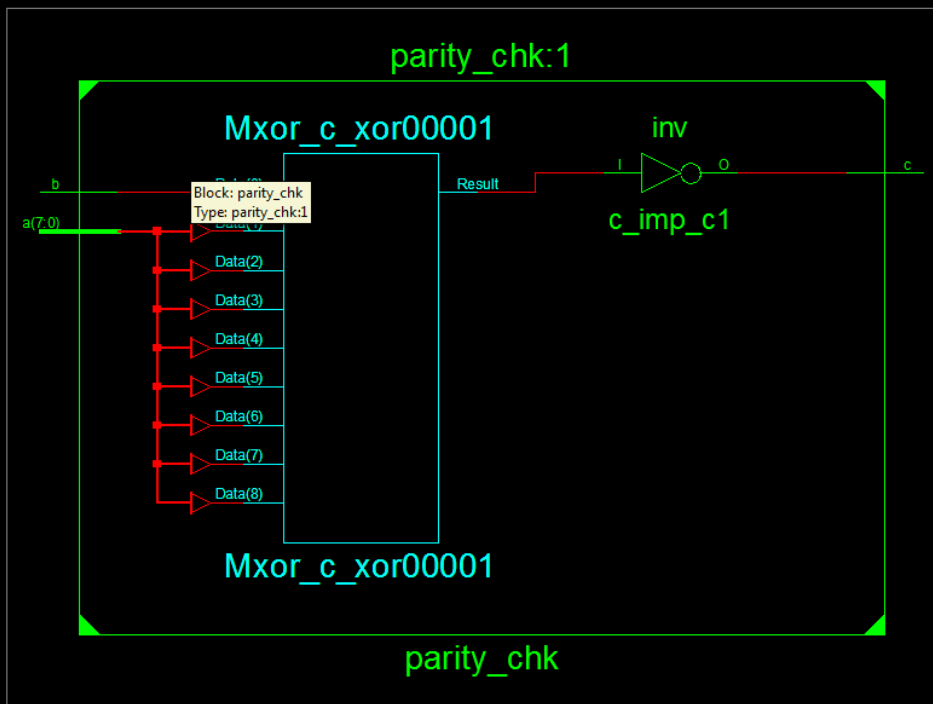

TEST BENCH :

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
ENTITY s1_ttb IS
END s1_ttb;

ARCHITECTURE behavior OF s1_ttb IS
  COMPONENT parity_chk
  PORT(
    a : IN std_logic_vector(7 downto 0);
    b : IN std_logic;
    c : OUT std_logic
  );
END COMPONENT;
```

```
signal a : std_logic_vector(7 downto 0) := (others => '0');
signal b : std_logic := '0';
```

```
signal c : std_logic;
```

```
BEGIN
```

```
uut: parity_chk PORT MAP (
```

```
a => a,  
b => b,  
c => c  
);
```

```
stim_proc: process  
begin
```


```
    a<="00000000";  
wait for 50 ns;  
a <="00001100";  
wait for 50 ns;  
a <="10010000";  
wait for 50 ns;  
a <="10001001";  
wait for 50 ns;  
a <="11010011";  
wait for 50 ns;  
a <="00001000";  
wait for 50 ns;  
a<="11011000";  
wait for 50 ns;
```

```
-- insert stimulus here
```

```
wait;  
end process;
```

```
END;
```

Simulation –

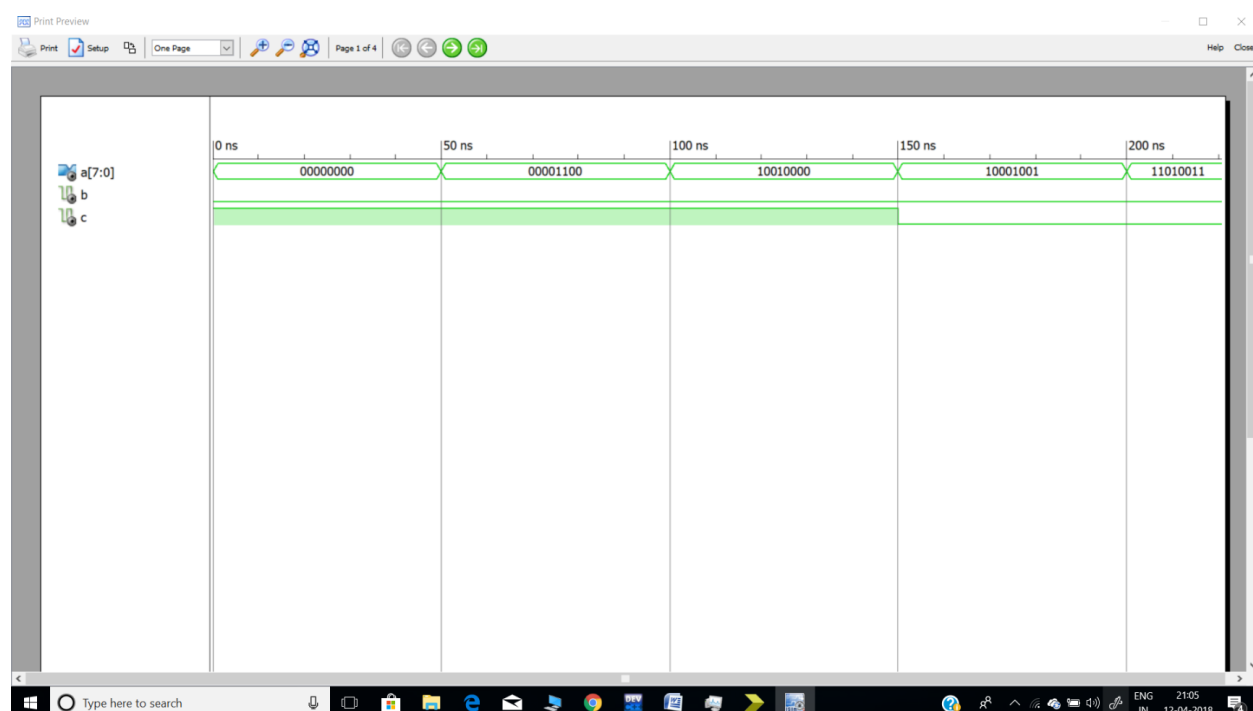

c.) Design a top level module called parity and use the previously designed two modules as components to check whether the functionality of the two modules are in synchronization or not.

VHDL MODULE:

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--use IEEE.NUMERIC_STD.ALL;

-- Uncomment the following library declaration if instantiating
-- any Xilinx primitives in this code.
--library UNISIM;
--use UNISIM.VComponents.all;

entity parity is
    Port ( a : in  STD_LOGIC_VECTOR (7 downto 0);
          b : out STD_LOGIC);
end parity;

architecture Structural of parity is

    component parity_gen is
        Port ( a : in  STD_LOGIC_VECTOR (7 downto 0);
              b : out STD_LOGIC);
    end component;

    component parity_chk is
        Port ( a : in  STD_LOGIC_VECTOR (7 downto 0);
              b : in  STD_LOGIC;
              c : out STD_LOGIC);
    end component;


    signal t1 : std_logic := '0';

begin

    x1 : parity_gen port map(a,t1);
    x2 : parity_chk port map(a,t1,b);

end Structural;
```

RTL Schematic –

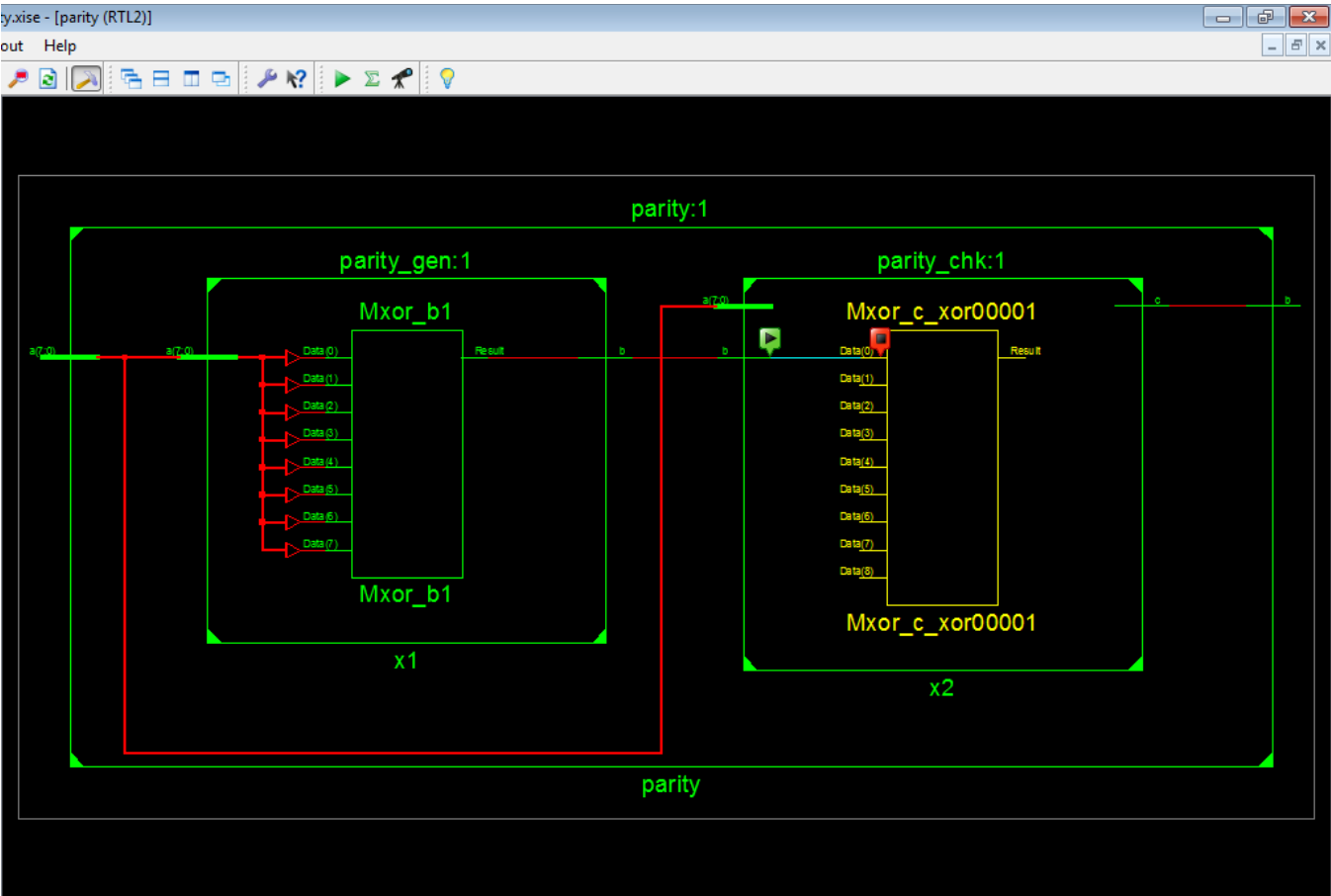

TEST BENCH :

```
LIBRARY ieee;  
USE ieee.std_logic_1164.ALL;
```

```
ENTITY TEST IS  
END TEST;
```

```
ARCHITECTURE behavior OF TEST IS
```

```
    COMPONENT parity  
    PORT(  
        a : IN  std_logic_vector(0 to 7);  
        b : OUT std_logic_vector(0 to 8);  
        b_error: OUT std_logic  
    );  
END COMPONENT;
```

```
    signal a: std_logic_vector(0 to 7) := (others => '0');
```

```
    signal b : std_logic_vector(0 to 8);  
    signal b_error : std_logic;
```

```
BEGIN
```

```
    uut: parity PORT MAP (  
        a=> a,  
        b => b,  
        b_error => b_error  
    );
```




```

stim_proc: process
begin
    a<="00001100";
wait for 50 ns;
a<="10001000";
wait for 50 ns;
a<="01100100";
wait for 50 ns;
a <="00010100";
wait for 50 ns;
a <="11100000";
wait for 50 ns;
a <="01110000";
wait for 50 ns;
a <="10100101";
wait for 50 ns;
    wait;
end process;

END;

```

Simulation –

 

4.)The diagram of a barrel shifter is shown below: The circuit must shift the input vector of size 8 either 0 or 1 position to the left. When actually shifted (shift = 1), the LSB bit must be filled with '0'. If shift = 0, then out=in; else, if shift = 1, then out(0)='0' and out(i)=in(i-1), for $1 \leq i \leq 7$. Write a concurrent code for this circuit and verify its behavior.

VHDL MODULE:

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

```

```
-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--use IEEE.NUMERIC_STD.ALL;

-- Uncomment the following library declaration if instantiating
-- any Xilinx primitives in this code.
--library UNISIM;
--use UNISIM.VComponents.all;
```


entity barrel is

```
Port ( i : in STD_LOGIC_VECTOR (7 downto 0);
      shift : in STD_LOGIC;
      o : out STD_LOGIC_VECTOR (7 downto 0));
end barrel;
```

architecture Behavioral of barrel is

```
begin
mux0 : entity work.moxx port map(i0=>'0',i1=>i(0),s=>shift,o=>o(0));
mux1 : entity work.moxx port map(i0=>i(0),i1=>i(1),s=>shift,o=>o(1));
mux2 : entity work.moxx port map(i0=>i(1),i1=>i(2),s=>shift,o=>o(2));
mux3 : entity work.moxx port map(i0=>i(2),i1=>i(3),s=>shift,o=>o(3));
mux4 : entity work.moxx port map(i0=>i(3),i1=>i(4),s=>shift,o=>o(4));
mux5 : entity work.moxx port map(i0=>i(4),i1=>i(5),s=>shift,o=>o(5));
mux6 : entity work.moxx port map(i0=>i(5),i1=>i(6),s=>shift,o=>o(6));
mux7 : entity work.moxx port map(i0=>i(6),i1=>i(7),s=>shift,o=>o(7));
end Behavioral;
```

RTL Schematic –

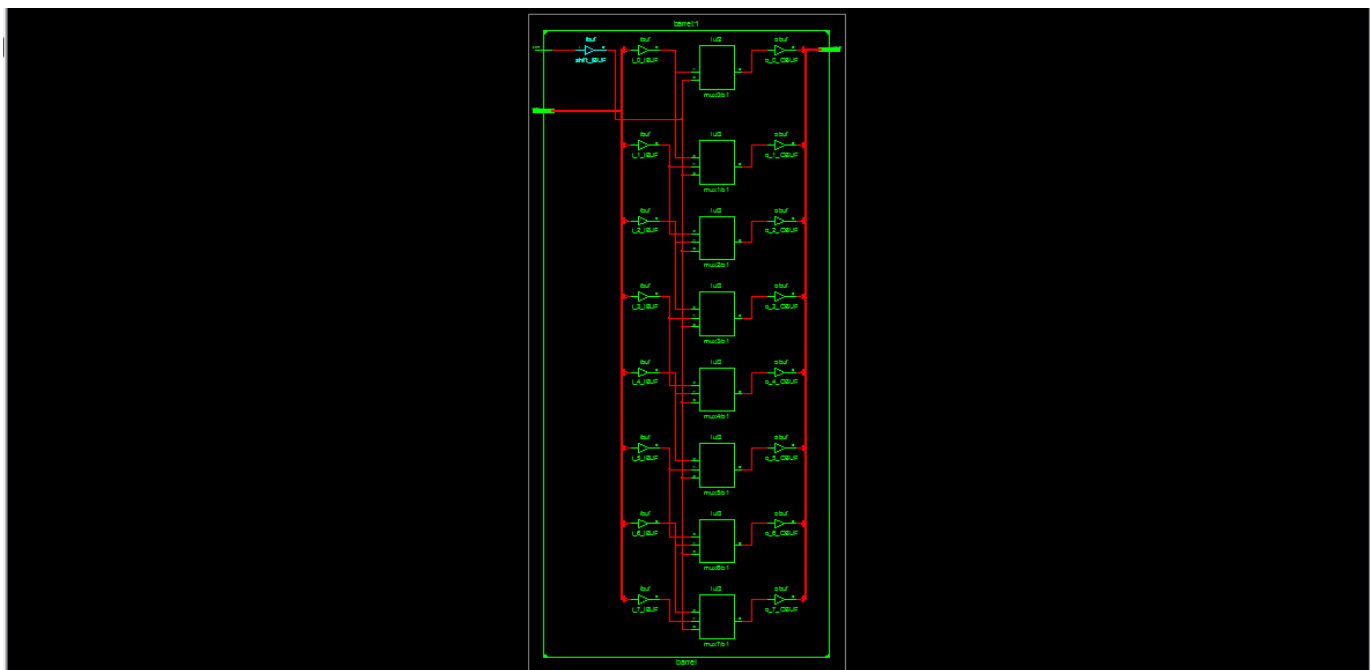

TEST BENCH :

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
```

```
-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--USE ieee.numeric_std.ALL;
```

```
ENTITY test IS
END test;
```

```
ARCHITECTURE behavior OF test IS
```

```
-- Component Declaration for the Unit Under Test (UUT)
```

```
COMPONENT ALU_m
PORT(
    a : IN  std_logic_vector(15 downto 0);
    b : IN  std_logic_vector(15 downto 0);
    sel : IN  std_logic_vector(3 downto 0);
    cin : IN  std_logic;
    y : OUT std_logic_vector(15 downto 0)
);
END COMPONENT;
```

```
--Inputs
signal a : std_logic_vector(15 downto 0) := (others => '0');
signal b : std_logic_vector(15 downto 0) := (others => '0');
signal sel : std_logic_vector(3 downto 0) := (others => '0');
signal cin : std_logic := '0';
```

```
--Outputs
signal y : std_logic_vector(15 downto 0);
-- No clocks detected in port list. Replace <clock> below with
-- appropriate port name
```

```
--constant <clock>_period : time := 10 ns;
```

```
BEGIN
```

```
-- Instantiate the Unit Under Test (UUT)
```

```
uut: ALU_m PORT MAP (
    a => a,
    b => b,
    sel => sel,
    cin => cin,
    y => y
);
```

```
-- Clock process definitions
--<clock>_process :process
--begin
--<clock><= '0';
--wait for <clock>_period/2;
--<clock><= '1';
--wait for <clock>_period/2;
--end process;
```

```
-- Stimulus process
stim_proc: process
begin
    -- hold reset state for 100 ns.
    --wait for 100 ns;
```

```
--wait for <clock>_period*10;
```

```
-- insert stimulus here
a<="1000111000110110";
b<="0010011101001101";
cin<='0';
sel<="0000";
wait for 20 ns;
```

```
sel<="0001";
wait for 20 ns;
sel<="0010";
wait for 20 ns;
sel<="0011";
wait for 20 ns;
sel<="0100";
wait for 20 ns;
sel<="0101";
wait for 20 ns;
sel<="0110";
wait for 20 ns;
    sel<="0111";
wait for 20 ns;
sel<="1000";
wait for 20 ns;
sel<="1001";
wait for 20 ns;
sel<="1010";
wait for 20 ns;
    sel<="1011";
wait for 20 ns;
sel<="1111";
wait for 20 ns;
    wait;
end process;
```

END;

Simulation –



5.) Design an 16 bit ALU (Arithmetic Logic Unit) as shown in the following figure and verify it's behavior with simulation.

The arithmetic and logical operations that are supported are listed below:

Unit	Function	Sel
Arithmetic	Transfer a	0000
	Increment a	0001
	Decrement a	0010
	Transfer b	0011
	Increment b	0100
	Decrement b	0101
	Add a and b	0110
	Add a and b with carry	0111
Logical	Complement a	1000
	Complement b	1001
	AND	1010
	OR	1011
	NAND	1100
	NOR	1101
	XOR	1110
	XNOR	1111

VHDL MODULE:

MUX:

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--use IEEE.NUMERIC_STD.ALL;

-- Uncomment the following library declaration if instantiating
-- any Xilinx primitives in this code.
--library UNISIM;
--use UNISIM.VComponents.all;

entity mux is
  Port ( i0 : in  STD_LOGIC_VECTOR (15 downto 0);
        i1 : in  STD_LOGIC_VECTOR (15 downto 0);
        y : out STD_LOGIC_VECTOR (15 downto 0);
        sel : in  STD_LOGIC_VECTOR (3 downto 0));
end mux;

architecture Behavioral of mux is
```

```
begin
y<= i0 when sel(3) = '0' else
i1 when sel(3) = '1' ;
```

end Behavioral;

Logic Unit:

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
use IEEE.NUMERIC_STD.ALL;
use ieee.std_logic_unsigned.all;
-- Uncomment the following library declaration if instantiating
-- any Xilinx primitives in this code.
--library UNISIM;
--use UNISIM.VComponents.all;
```

```
entity logic_unit is
  Port ( sel : in  STD_LOGIC_VECTOR (3 downto 0);
        a : in  STD_LOGIC_VECTOR (15 downto 0);
        b : in  STD_LOGIC_VECTOR (15 downto 0);
        o : out STD_LOGIC_VECTOR (15 downto 0));
end logic_unit;
```

architecture Behavioral of logic_unit is

```
begin
o<= not a when sel= "1000" else
not b when sel= "1001" else
a and b when sel="1010" else
a or b when sel="1011" else
a nand b when sel="1100" else
a nor b when sel="1101" else
a xor b when sel="1110" else
a xnor b when sel="1111";
```

end Behavioral;

Arithmetic Unit:

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
use IEEE.NUMERIC_STD.ALL;
use ieee.std_logic_unsigned.all;
-- Uncomment the following library declaration if instantiating
-- any Xilinx primitives in this code.
--library UNISIM;
--use UNISIM.VComponents.all;
```

```
entity arithmetic is
  Port ( a : in  STD_LOGIC_VECTOR (15 downto 0);
```

```

        b : in  STD_LOGIC_VECTOR (15 downto 0);
        sel : in  STD_LOGIC_VECTOR (3 downto 0);
        o : out STD_LOGIC_VECTOR (15 downto 0);
    cin: in STD_LOGIC);
end arithmetic;

```

architecture Behavioral of arithmetic is

```

begin
o<= a when sel= "0000" else
a+1 when sel= "0001" else
a-1 when sel="0010" else
b when sel="0011" else
b+1 when sel="0100" else
b-1 when sel="0101" else
a+b when sel="0110" else
a + b + cin when sel="0111";

```

end Behavioral;

ALU:

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

```

```

-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
use IEEE.NUMERIC_STD.ALL;
use ieee.std_logic_unsigned.all;
-- Uncomment the following library declaration if instantiating
-- any Xilinx primitives in this code.
--library UNISIM;
--use UNISIM.VComponents.all;

```

```

entity ALU_m is
    Port ( a : in  STD_LOGIC_VECTOR (15 downto 0);
          b : in  STD_LOGIC_VECTOR (15 downto 0);
          sel : in  STD_LOGIC_VECTOR (3 downto 0);
          cin : in  STD_LOGIC;
          y : out STD_LOGIC_VECTOR (15 downto 0));
end ALU_m;

```

```

architecture Behavioral of ALU_m is
signal o1 : std_logic_vector(15 downto 0);
signal o2 : std_logic_vector(15 downto 0);
begin
ar : entity work.arithmetic port map(
a=>a,
b=>b,
sel=> sel,
cin=>cin,
o=>o1);
log : entity work.logic_unit port map(
a=>a,
b=>b,
sel=>sel,
--cin=>cin,


```

```

o=>o2);
moxxie : entity work.mux port map(
i0=> o1,
i1=> o2,
sel=>sel,
y=>y);
end Behavioral;

```

RTL Schematic –

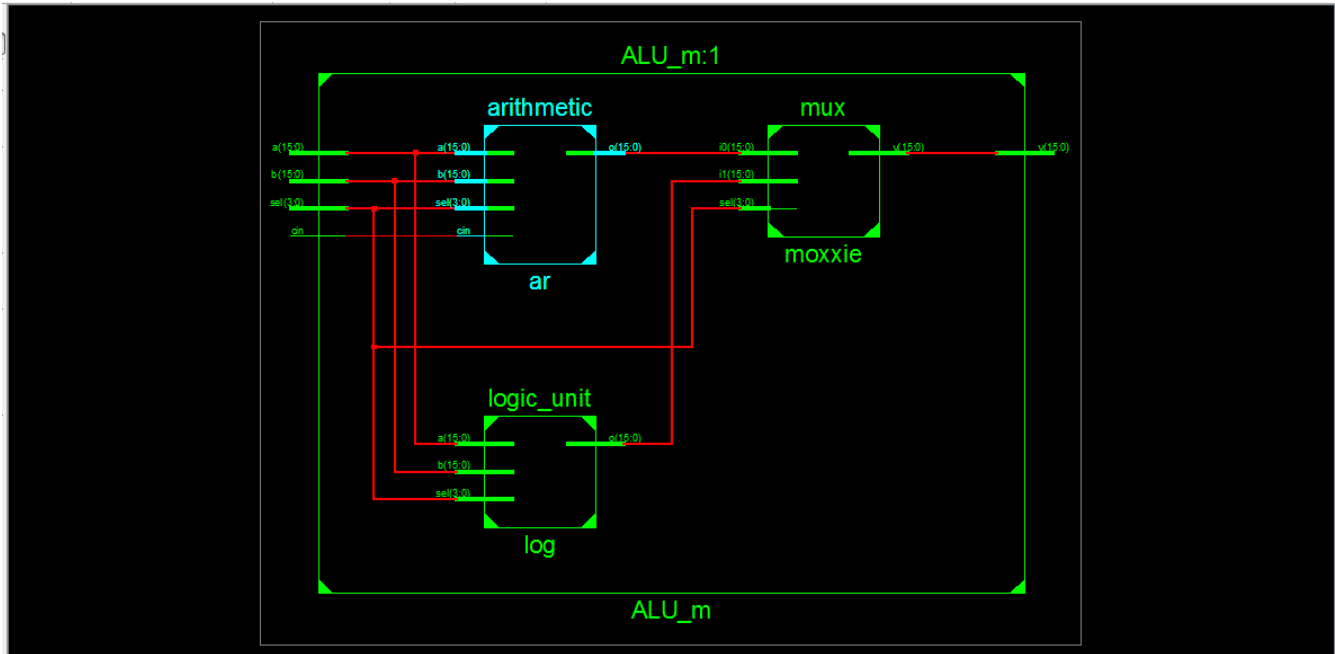

TEST BENCH :

```

LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

```

```

-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--USE ieee.numeric_std.ALL;

```

```

ENTITY test IS
END test;

```

ARCHITECTURE behavior OF test IS

```

-- Component Declaration for the Unit Under Test (UUT)

```

```

COMPONENT ALU_m
PORT(
  a : IN std_logic_vector(15 downto 0);
  b : IN std_logic_vector(15 downto 0);
  sel : IN std_logic_vector(3 downto 0);
  cin : IN std_logic;
  y : OUT std_logic_vector(15 downto 0)
);
END COMPONENT;

```


--Inputs

signal a : std_logic_vector(15 downto 0) := (others => '0');

signal b : std_logic_vector(15 downto 0) := (others => '0');

signal sel : std_logic_vector(3 downto 0) := (others => '0');

signal cin : std_logic := '0';

--Outputs

signal y : std_logic_vector(15 downto 0);

-- No clocks detected in port list. Replace <clock> below with

-- appropriate port name

--constant <clock>_period : time := 10 ns;

BEGIN

-- Instantiate the Unit Under Test (UUT)

uut: ALU_m PORT MAP (

a => a,

b => b,

sel => sel,

cin => cin,

y => y

);

-- Clock process definitions

--<clock>_process :process

--begin

--<clock><= '0';

--wait for <clock>_period/2;

--<clock><= '1';

--wait for <clock>_period/2;

--end process;

-- Stimulus process

stim_proc: process

begin

-- hold reset state for 100 ns.

--wait for 100 ns;

--wait for <clock>_period*10;

-- insert stimulus here

a<="1000111000110110";

b<="0010011101001101";

cin<='0';

sel<="0000";

wait for 20 ns;

sel<="0001";

wait for 20 ns;

sel<="0010";

wait for 20 ns;

sel<="0011";

wait for 20 ns;

sel<="0100";

wait for 20 ns;

```
sel<="0101";
wait for 20 ns;
sel<="0110";
wait for 20 ns;
    sel<="0111";
wait for 20 ns;
sel<="1000";
wait for 20 ns;
sel<="1001";
wait for 20 ns;
sel<="1010";
wait for 20 ns;
    sel<="1011";
wait for 20 ns;
sel<="1111";
wait for 20 ns;
    wait;
end process;

END;
```

Simulation –

