# IT 451: Computer Organization and Architecture (Sessional)

Name – Anupam Sanidhya

Enrolment number – 510817049

Roll number – 42 (Hy)

## **Assignment 5**

# 32 bit ALU -

#### **VHDL MODULE:**

```
begin
```

```
process(CLK)
begin
       if(rising_edge(CLK)) then
              if(unsigned(Set)=0) then
                     temp<=A;
              elsif(unsigned(Set)=1) then
                     temp <= A + x"1";
              elsif(unsigned(Set)=2) then
                     temp<=A-x"1";
              elsif(unsigned(Set)=3) then
                     temp<=B;
              elsif(unsigned(Set)=4) then
                     temp \le B+x"1";
              elsif(unsigned(Set)=5) then
                     temp \le B-x"1";
              elsif(unsigned(Set)=6) then
                     temp<=A+B;
              elsif(unsigned(Set)=7) then
                     temp<=A+B+carry;
              elsif(unsigned(Set)=8) then
                     temp<= not A;
              elsif(unsigned(Set)=9) then
                     temp<= not B;
              elsif(unsigned(Set)=10) then
                     temp<= A and B;
              elsif(unsigned(Set)=11) then
```

 $temp \le A \text{ or } B$ ;

```
elsif(unsigned(Set)=12) then
temp<= A nand B;
elsif(unsigned(Set)=13) then
temp<= A nor B;
elsif(unsigned(Set)=14) then
temp<= A xor B;
elsif(unsigned(Set)=15) then
temp<= A xnor B;
end if;
end process;
O<=temp;
end Behavioral;
```

#### **TEST BENCH:**

```
LIBRARY ieee;

USE ieee.std_logic_1164.ALL;

USE ieee.std_logic_UNSIGNED.ALL;

USE ieee.numeric_std.ALL;
```

ENTITY ALU\_32bit\_test IS
END ALU\_32bit\_test;

ARCHITECTURE behavior OF ALU\_32bit\_test IS

```
COMPONENT ALU_32bit
PORT(
   A: IN std_logic_vector(31 downto 0);
   B: IN std_logic_vector(31 downto 0);
   CLK: IN std_logic;
   carry: IN std_logic;
   Set: IN std_logic_vector(3 downto 0);
   O: OUT std_logic_vector(31 downto 0)
   );
END COMPONENT;
--Inputs
signal A: std_logic_vector(31 downto 0) := (others => '0');
signal B: std_logic_vector(31 downto 0) := (others => '0');
signal CLK : std_logic := '0';
signal carry: std_logic := '0';
signal Set: std_logic_vector(3 downto 0) := (others => '0');
     --Outputs
signal O: std_logic_vector(31 downto 0);
-- Clock period definitions
constant CLK_period : time := 10 ns;
```

-- Component Declaration for the Unit Under Test (UUT)

```
uut: ALU_32bit PORT MAP (
    A \Rightarrow A,
    B \Rightarrow B,
    CLK => CLK,
    carry => carry,
    Set => Set,
    O => 0
   );
-- Clock process definitions
CLK_process :process
begin
             CLK <= '0';
             wait for CLK_period/2;
             CLK <= '1';
             wait for CLK_period/2;
end process;
-- Stimulus process
stim_proc: process
begin
 -- hold reset state for 100 ns.
 wait for 100 ns;
 wait for CLK_period;
```


-- Instantiate the Unit Under Test (UUT)

```
Set<="0000";
wait for CLK_period;
Set<="0001";
wait for CLK_period;
Set<="0010";
wait for CLK_period;
Set<="0011";
wait for CLK_period;
Set<="0100";
wait for CLK_period;
Set<="0101":
wait for CLK_period;
Set<="0110";
wait for CLK_period;
```


```
Set<="0111";
wait for CLK_period;
Set<="1000";
wait for CLK_period;
Set<="1001";
wait for CLK_period;
Set<="1010";
wait for CLK_period;
Set<="1011";
wait for CLK_period;
Set<="1100":
wait for CLK_period;
Set<="1101";
wait for CLK_period;
```

#### RTL Schematic -

END;

 

### Simulation -

 

=======================================	========			==========
===				
* De:	sign Summa	ary	*	
===	=======			
Top Level Output File	e Name	: ALU_32bit.ngc		
Primitive and Black Bo	ox Usage:			

# BELS : 796

# GND :1

# INV : 64

# LUT1 : 95

# LUT2 : 33

# LUT4 : 64

# LUT6 : 64

# MUXCY : 186

# MUXF7 : 64

# MUXF8 : 32

# VCC : 1

# XORCY : 192

# FlipFlops/Latches : 32

# FD : 32

# Clock Buffers : 1

# BUFGP : 1

# IO Buffers : 101

# IBUF : 69

# OBUF : 32

Device utilization summary:

\_\_\_\_\_

Selected Device: 6slx4tqg144-3

Slice Logic Utilization:

Number of Slice LUTs: 320 out of 2400 13%

Number used as Logic: 320 out of 2400 13%

Slice Logic Distribution:

Number of LUT Flip Flop pairs used: 320

Number with an unused Flip Flop: 320 out of 320 100%

Number with an unused LUT: 0 out of 320 0%

Number of fully used LUT-FF pairs: 0 out of 320 0%

Number of unique control sets: 1

IO Utilization:

Number of IOs: 102

Number of bonded IOBs: 102 out of 102 100%

IOB Flip Flops/Latches: 32

Specific Feature Utilization:

Number of BUFG/BUFGCTRLs: 1 out of 16 6%

### 16 bit ALU -

#### **VHDL MODULE:**


```
MUX:
library IEEE;
use IEEE.STD LOGIC 1164.ALL;
-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--use IEEE.NUMERIC STD.ALL;
-- Uncomment the following library declaration if instantiating
-- any Xilinx primitives in this code.
--library UNISIM;
--use UNISIM.VComponents.all;
entity mux is
  Port (i0: in STD_LOGIC_VECTOR (15 downto 0);
      i1: in STD LOGIC VECTOR (15 downto 0);
     y: out STD_LOGIC_VECTOR (15 downto 0);
      sel: in STD LOGIC VECTOR (3 downto 0));
end mux;
architecture Behavioral of mux is
begin
y \le i0 when sel(3) = '0' else
i1 when sel(3) = '1';
end Behavioral;
       Logic Unit:
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
use IEEE.NUMERIC_STD.ALL;
use ieee.std logic unsigned.all;
-- Uncomment the following library declaration if instantiating
-- any Xilinx primitives in this code.
--library UNISIM;
```

```
--use UNISIM.VComponents.all;
entity logic unit is
  Port ( sel : in STD_LOGIC_VECTOR (3 downto 0);
     a: in STD LOGIC VECTOR (15 downto 0);
     b: in STD LOGIC VECTOR (15 downto 0);
     o: out STD_LOGIC_VECTOR (15 downto 0));
end logic unit;
architecture Behavioral of logic_unit is
begin
o<= not a when sel= "1000" else
not b when sel= "1001" else
a and b when sel="1010" else
a or b when sel="1011" else
a nand b when sel="1100" else
a nor b when sel="1101" else
a xor b when sel="1110" else
a xnor b when sel="1111";
end Behavioral;
       Arithmetic Unit:
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
use IEEE.NUMERIC_STD.ALL;
use ieee.std logic unsigned.all;
-- Uncomment the following library declaration if instantiating
-- any Xilinx primitives in this code.
--library UNISIM;
--use UNISIM.VComponents.all;
entity arithmetic is
  Port (a:in STD_LOGIC_VECTOR (15 downto 0);
     b: in STD LOGIC VECTOR (15 downto 0);
     sel: in STD LOGIC VECTOR (3 downto 0);
     o: out STD_LOGIC_VECTOR (15 downto 0);
 cin: in STD LOGIC);
end arithmetic;
architecture Behavioral of arithmetic is
```

```
begin
o<= a when sel= "0000" else
a+1 when sel= "0001" else
a-1 when sel="0010" else
b when sel="0011" else
b+1 when sel="0100" else
b-1 when sel="0101" else
a+b when sel="0110" else
a + b + cin when sel="0111";
end Behavioral;
       ALU:
library IEEE;
use IEEE.STD LOGIC 1164.ALL;
-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
use IEEE.NUMERIC STD.ALL;
use ieee.std_logic_unsigned.all;
-- Uncomment the following library declaration if instantiating
-- any Xilinx primitives in this code.
--library UNISIM;
--use UNISIM.VComponents.all;
entity ALU_m is
  Port (a:in STD LOGIC VECTOR (15 downto 0);
     b: in STD LOGIC VECTOR (15 downto 0);
     sel: in STD_LOGIC_VECTOR (3 downto 0);
     cin: in STD_LOGIC;
     y: out STD LOGIC VECTOR (15 downto 0));
end ALU_m;
architecture Behavioral of ALU m is
signal o1 : std logic vector(15 downto 0);
signal o2 : std_logic_vector(15 downto 0);
ar: entity work.arithmetic port map(
a=>a,
b=>b.
sel=> sel,
cin=>cin,
log: entity work.logic_unit port map(
a=>a,
b=>b,
```

```
sel=>sel,
--cin=>cin,
o=>o2);
moxxie : entity work.mux port map(
i0=> o1,
i1=> o2,
sel=>sel,
y=>y);
end Behavioral;
```

### **RTL Schematic –**

 

#### **TEST BENCH:**

LIBRARY ieee; USE ieee.std\_logic\_1164.ALL;

- -- Uncomment the following library declaration if using
- -- arithmetic functions with Signed or Unsigned values
- --USE ieee.numeric\_std.ALL;

ENTITY test IS END test;

ARCHITECTURE behavior OF test IS

```
-- Component Declaration for the Unit Under Test (UUT)
  COMPONENT ALU m
  PORT(
    a: IN std logic vector(15 downto 0);
    b: IN std logic vector(15 downto 0);
    sel: IN std_logic_vector(3 downto 0);
    cin: IN std logic;
    y: OUT std_logic_vector(15 downto 0)
    );
  END COMPONENT;
 --Inputs
 signal a : std logic vector(15 downto 0) := (others => '0');
 signal b : std_logic_vector(15 downto 0) := (others => '0');
 signal sel : std_logic_vector(3 downto 0) := (others => '0');
 signal cin : std_logic := '0';
 --Outputs
 signal y: std_logic_vector(15 downto 0);
 -- No clocks detected in port list. Replace <clock> below with
 -- appropriate port name
 --constant <clock>_period : time := 10 ns;
BEGIN
-- Instantiate the Unit Under Test (UUT)
 uut: ALU m PORT MAP (
     a => a,
     b => b,
     sel => sel,
     cin => cin,
     y => y
    );
 -- Clock process definitions
 --<clock>_process :process
 --begin
--<clock><= '0';
--wait for <clock>_period/2;
--<clock><= '1';
--wait for <clock> period/2;
 --end process;
```

```
-- Stimulus process
 stim proc: process
   -- hold reset state for 100 ns.
   --wait for 100 ns;
   --wait for <clock>_period*10;
   -- insert stimulus here
a<="1000111000110110";
b<="0010011101001101";
cin<='0';
sel<="0000";
wait for 20 ns;
sel<="0001";
wait for 20 ns;
sel<="0010";
wait for 20 ns;
sel<="0011";
wait for 20 ns;
sel<="0100";
wait for 20 ns;
sel<="0101";
wait for 20 ns;
sel<="0110";
wait for 20 ns;
   sel<="0111";
wait for 20 ns;
sel<="1000";
wait for 20 ns;
sel<="1001";
wait for 20 ns;
sel<="1010";
wait for 20 ns;
   sel<="1011";
wait for 20 ns;
sel<="1111";
wait for 20 ns;
   wait;
 end process;
END;
```

## Simulation –

* p*		14 14	14			1,000.000 ns		
Name	Value	0 ns	200 ns	400 ns	600 ns	800 ns		
► a[15:0]	1000111000110110			1000111000110110				
▶ □ b[15:0]	0010011101001101			0010011101001101				
► =6 sel[3:0]	1111				1111			
16 cin	0							
y[15:0]	0101011010000100			01010	11010000100			
		XI: 1,000,000 ns						