

IT 451: Computer Organization and Architecture (Sessional)

Name – Anupam Sanidhya

Enrolment number – 510817049

Roll number – 42 (Hy)

Assignment 3

Question 1

VHDL MODULE :

```
library IEEE;

use IEEE.STD_LOGIC_1164.ALL;

use IEEE.NUMERIC_STD.ALL;

use ieee.std_logic_unsigned.all;

entity convertor is

Port ( ip : in  STD_LOGIC_VECTOR (3 downto 0);

sel : in  STD_LOGIC_VECTOR (2 downto 0);

op : out  STD_LOGIC_VECTOR (3 downto 0));

end convertor;

architecture Behavioral of convertor is

signal bin2ex3 : std_logic_vector(3 downto 0);

signal ex32bin : std_logic_vector(3 downto 0);

begin
```

```
bin2ex3<=ip+3;
ex32bin<=ip-3;
op(0) <= ip(0) xor ip(1)
    when sel="000" else --binary2gray
ip(0) xor ip(1) xor ip(2) xor ip(3)
    when sel="001" else
bin2ex3(0)
    when sel="010" else
ex32bin(0) when sel="011"; -- else
```

```
op(1) <=ip(2) xor ip(1)
    when sel="000" else
ip(2) xor ip(1) xor ip(3)
    when sel="001" else
bin2ex3(1)
    when sel="010" else
ex32bin(1)
    when sel="011" ;
```

```
op(2) <=ip(3) xor ip(2)
    when sel="000" else
ip(3) xor ip(2)
    when sel="001" else
bin2ex3(2)
    when sel="010" else
ex32bin(2)
```

```

        when sel="011";

op(3) <=ip(3)

        when sel="000" else

ip(3)

        when sel="001" else

bin2ex3(3)

        when sel="010" else

ex32bin(3)

        when sel="011";

end Behavioral;

```

TEST BENCH :

```

LIBRARY ieee;

USE ieee.std_logic_1164.ALL;

-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--USE ieee.numeric_std.ALL;

ENTITY cnvrt_test IS

END cnvrt_test;

ARCHITECTURE behavior OF cnvrt_test IS

    -- Component Declaration for the Unit Under Test (UUT)

```

COMPONENT convertor

PORT(

ip : IN std_logic_vector(3 downto 0);

sel : IN std_logic_vector(2 downto 0);

op : OUT std_logic_vector(3 downto 0)

);

END COMPONENT;

--Inputs

signal ip : std_logic_vector(3 downto 0) := (others => '0');

signal sel : std_logic_vector(2 downto 0) := (others => '0');

--Outputs

signal op : std_logic_vector(3 downto 0);

-- No clocks detected in port list. Replace <clock> below with

-- appropriate port name

--constant <clock>_period : time := 10 ns;

BEGIN

-- Instantiate the Unit Under Test (UUT)

uut: convertor PORT MAP (

ip => ip,

sel => sel,

```

        op => op

    );

-- Clock process definitions
--

-- Stimulus process
stim_proc: process
begin
    -- hold reset state for 100 ns.
    -- wait for 100 ns;

    -- wait for <clock>_period*10;

    -- insert stimulus here

    ip<= "1000","1010" after 200 ns,"1110" after 300 ns, "1100" after 500 ns,"1001" after 700
ns;


    sel <= "000", "001" after 300 ns, "010" after 500 ns,"011" after 600 ns;

    wait;


end process;

END;
```

Simulation -

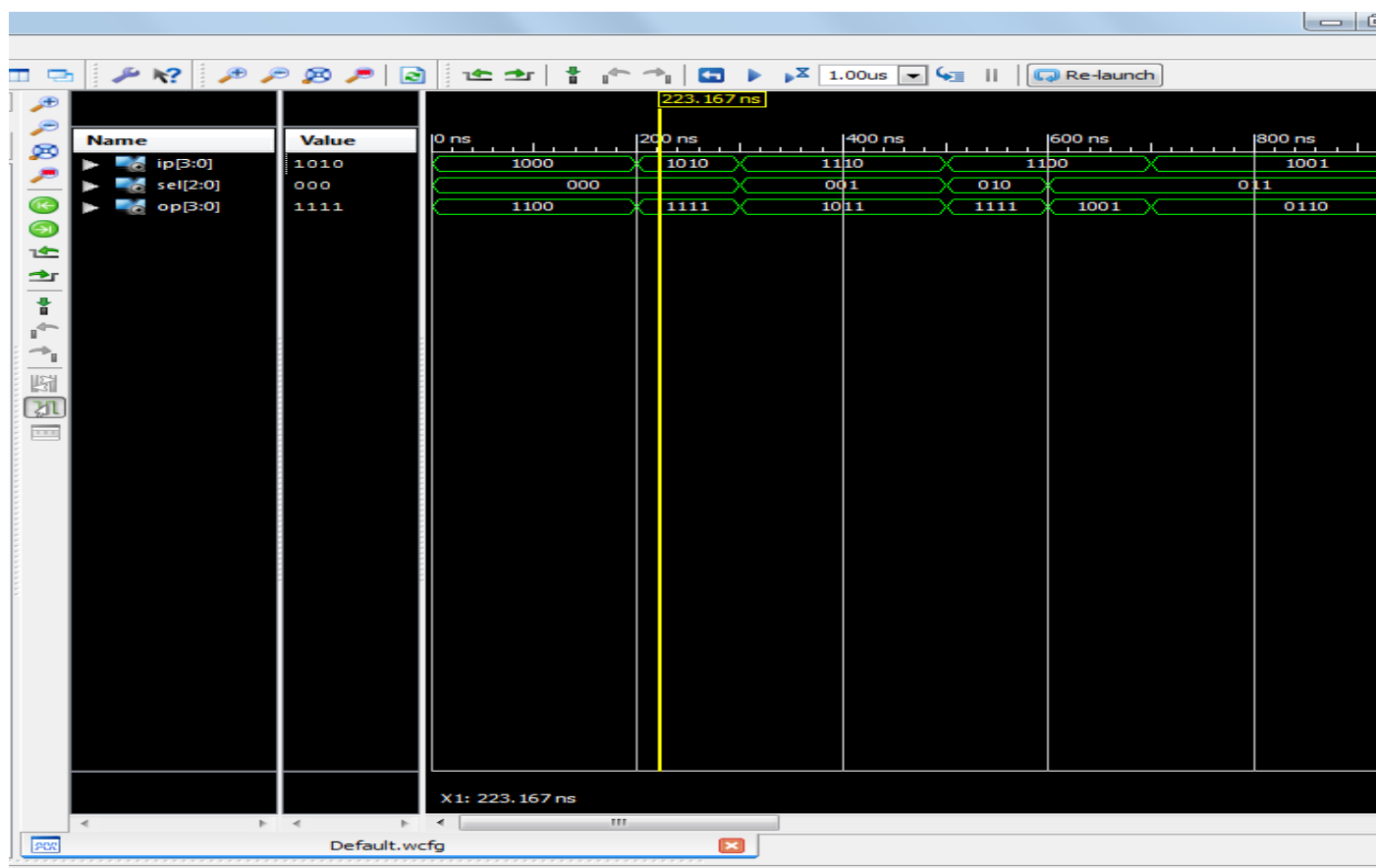

RTL Schematic –

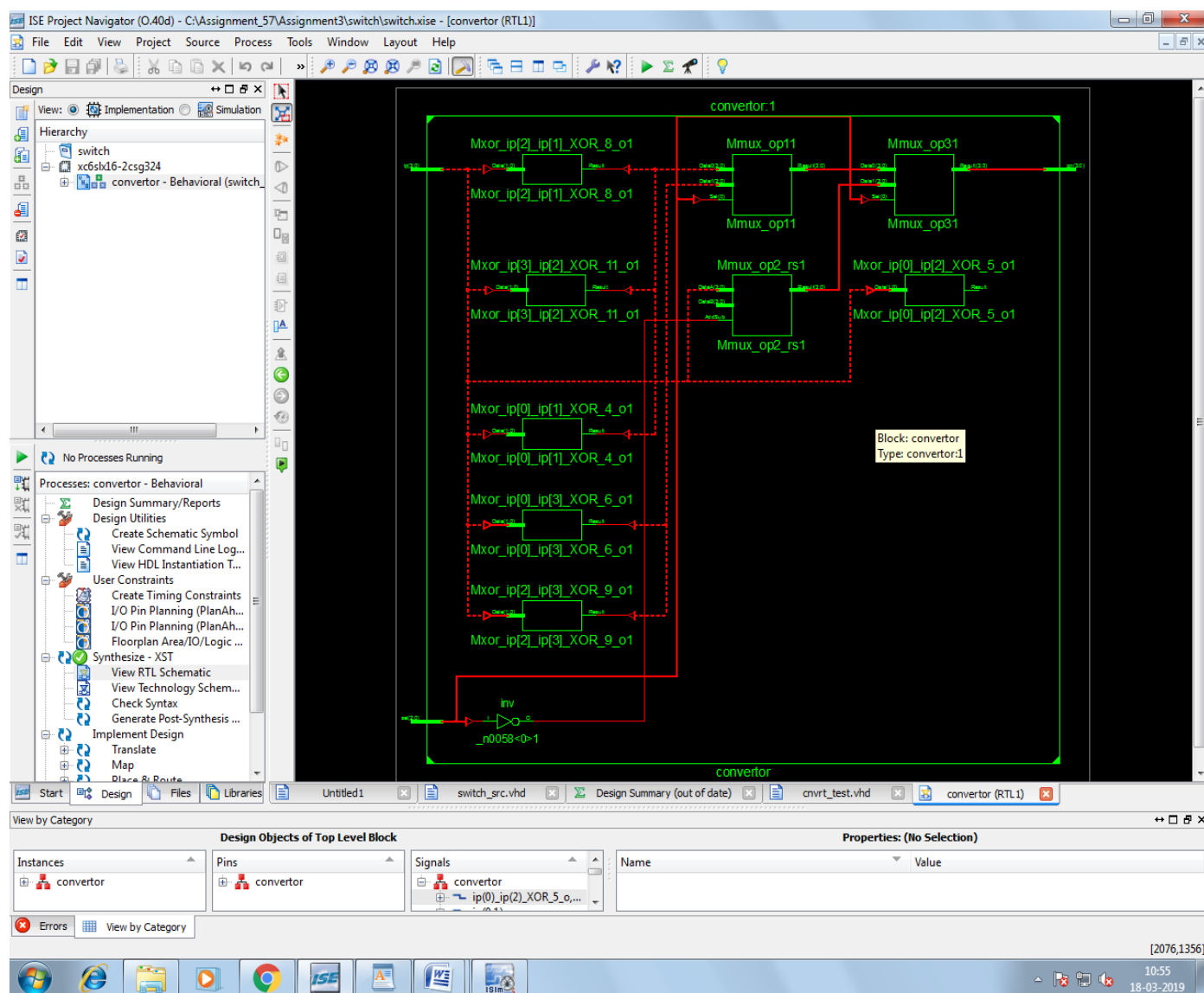

Question 2

VHDL MODULE :

```
library IEEE;

use IEEE.STD_LOGIC_1164.ALL;

use IEEE.NUMERIC_STD.ALL;

use ieee.STD_LOGIC_UNSIGNED.all;


-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--use IEEE.NUMERIC_STD.ALL;


-- Uncomment the following library declaration if instantiating
-- any Xilinx primitives in this code.
--library UNISIM;

--use UNISIM.VComponents.all;


entity mult is
```



```
Port ( a : in STD_LOGIC_VECTOR (7 downto 0);  
      b : in STD_LOGIC_VECTOR (7 downto 0);  
      c : out STD_LOGIC_VECTOR (15 downto 0));  
end mult;
```

architecture Behavioral of mult is

```
begin  
c<=a*b;
```

```
end Behavioral;
```

TEST BENCH :

```
LIBRARY ieee;  
USE ieee.std_logic_1164.ALL;
```

```
-- Uncomment the following library declaration if using  
-- arithmetic functions with Signed or Unsigned values  
--USE ieee.numeric_std.ALL;
```

```
ENTITY mult_test IS  
END mult_test;
```

```
ARCHITECTURE behavior OF mult_test IS
```

```
-- Component Declaration for the Unit Under Test (UUT)
```

COMPONENT mult

PORT(

a : IN std_logic_vector(7 downto 0);

b : IN std_logic_vector(7 downto 0);

c : OUT std_logic_vector(15 downto 0)

);

END COMPONENT;

--Inputs

signal a : std_logic_vector(7 downto 0) := "00000010";

signal b : std_logic_vector(7 downto 0) := "00000010";

--Outputs

signal c : std_logic_vector(15 downto 0);

-- No clocks detected in port list. Replace <clock> below with

-- appropriate port name

--constant <clock>_period : time := 10 ns;

BEGIN

-- Instantiate the Unit Under Test (UUT)

uut: mult PORT MAP (

a => a,

b => b,

c => c

```

);

-- Clock process definitions

-- <clock>_process :process

-- begin

        --<clock> <= '0';

        --      wait for <clock>_period/2;

        --      <clock> <= '1';

        --      wait for <clock>_period/2;

-- end process;


-- Stimulus process

stim_proc: process

begin

    -- hold reset state for 100 ns.

    wait for 100 ns;

        a<="00000011" after 200 ns;

        b<="00000001" after 100 ns;


    -- wait for <clock>_period*10;


    -- insert stimulus here

 

    wait;

end process;


```

END;

Simulation -



RTL Schematic –

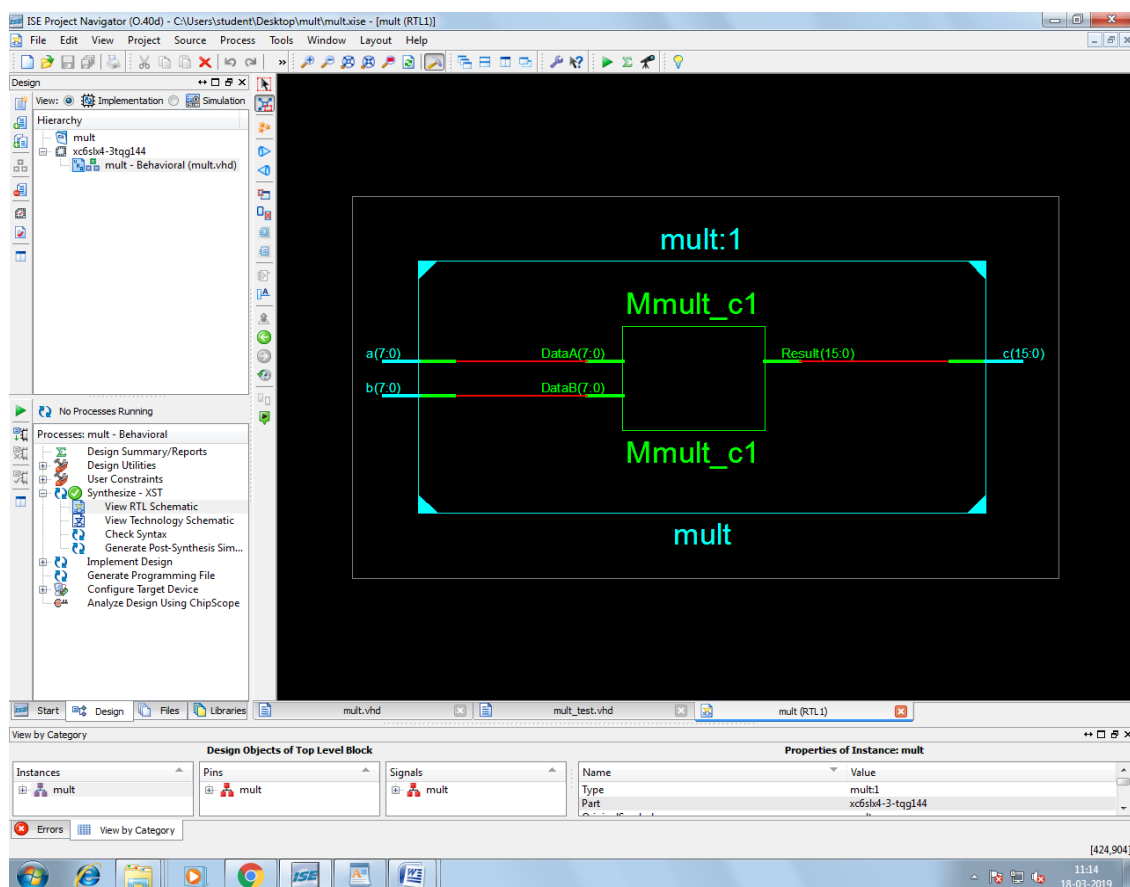

Question 3

VHDL MODULE :

```
library IEEE;

use IEEE.STD_LOGIC_1164.ALL;

use IEEE.NUMERIC_STD.ALL;

use IEEE.STD_LOGIC_UNSIGNED.ALL;


-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--use IEEE.NUMERIC_STD.ALL;


-- Uncomment the following library declaration if instantiating
-- any Xilinx primitives in this code.
--library UNISIM;
--use UNISIM.VComponents.all;


entity divider is
    Port ( dividend : in  STD_LOGIC_VECTOR (31 downto 0);
          divisor : in  STD_LOGIC_VECTOR (15 downto 0);
          quotient : out STD_LOGIC_VECTOR (31 downto 0));
end divider;


architecture Behavioral of divider is

begin

quotient <= std_logic_vector(to_signed(to_integer(signed(dividend) / signed(divisor)),32));


end Behavioral;
```

TEST BENCH :

```
LIBRARY ieee;
```

```
USE ieee.std_logic_1164.ALL;
```

```
-- Uncomment the following library declaration if using
```

```
-- arithmetic functions with Signed or Unsigned values
```

```
--USE ieee.numeric_std.ALL;
```

```
ENTITY divider_test IS
```

```
END divider_test;
```

```
ARCHITECTURE behavior OF divider_test IS
```

```
-- Component Declaration for the Unit Under Test (UUT)
```

```
COMPONENT divider
```

```
PORT(
```

```
    dividend : IN std_logic_vector(31 downto 0);
```

```
    divisor : IN std_logic_vector(15 downto 0);
```

```
    quotient : OUT std_logic_vector(31 downto 0)
```

```
);
```

```
END COMPONENT;
```

```
--Inputs
```

```
signal dividend : std_logic_vector(31 downto 0) := "00000000000000000000000000001000";
```

```
signal divisor : std_logic_vector(15 downto 0) := "0000000000000010";
```

```
--Outputs
```

```
signal quotient : std_logic_vector(31 downto 0);
```

```
-- No clocks detected in port list. Replace <clock> below with
```

```
-- appropriate port name
```

```
-- constant <clock>_period : time := 10 ns;
```

```
BEGIN
```

```
-- Instantiate the Unit Under Test (UUT)
```

```
uut: divider PORT MAP (
```

```
    dividend => dividend,
```

```
    divisor => divisor,
```

```
    quotient => quotient
```

```
);
```

```
-- Clock process definitions
```

```
-- <clock>_process :process
```

```
-- begin
```

```
    --    <clock> <= '0';
```

```
    --wait for <clock>_period/2;
```

```
--    <clock> <= '1';
```

```
    --    wait for <clock>_period/2;
```

```
-- end process;
```



```
-- Stimulus process

stim_proc: process

begin

    -- hold reset state for 100 ns.

    wait for 100 ns;


    -- wait for <clock>_period*10;

 

    -- insert stimulus here


    wait;

end process;


END;
```

Simulation -



RTL Schematic –

